

Brief Introduction to H/W Design

Table of Contents

- Circuit Elements
- Circuit Analysis
- Digital VS Analog
- Application of Elements
- Block Diagram
- Design H/W System

Elements

- Passive Elements
- Resistor(R), Capacitor(C), Inductor(L)
- Active Elements
- Diode, Transistor, Op-Amp etc.

Elements

- Resistor [Ω] = $\rho \frac{l}{S}$
- Series Connection : $R_{\text{tot}} = R_1 + R_2 + \dots + R_n$
- Parallel Connection : $R_{\text{tot}} = 1 / (1/R_1 + 1/R_2 + \dots + 1/R_n)$

Elements

- Inductor[H] = Wb/A
- 전류의 변화량에 비례해 전압을 유도 : $V=L\frac{di}{dt}$
- Series Connection : $L_{tot} = L1 + L2 + \dots + Ln$
- Parallel Connection : $L_{tot} = 1/(1/L1 + 1/L2 + \dots + 1/Ln)$

Elements

- Capacitor[F] = $\epsilon \frac{A}{d}$
- 전압의 변화량에 따라 전류가 발생 : $i = C \frac{dV}{dt}$
- Series Connection : $C_{tot} = 1 / (1/C_1 + 1/C_2 + \dots + 1/C_n)$
- Parallel Connection : $C_{tot} = C_1 + C_2 + \dots + C_n$


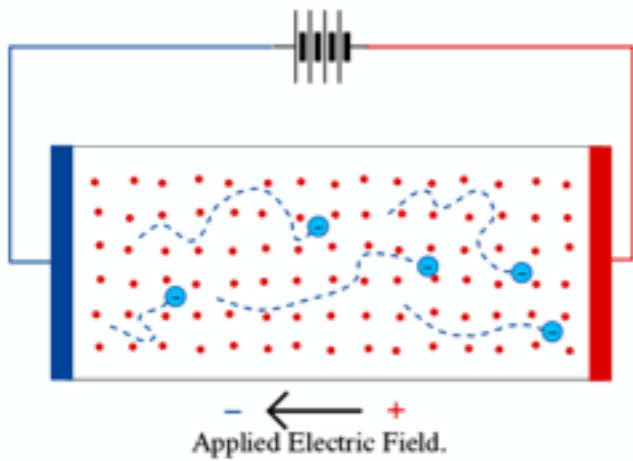
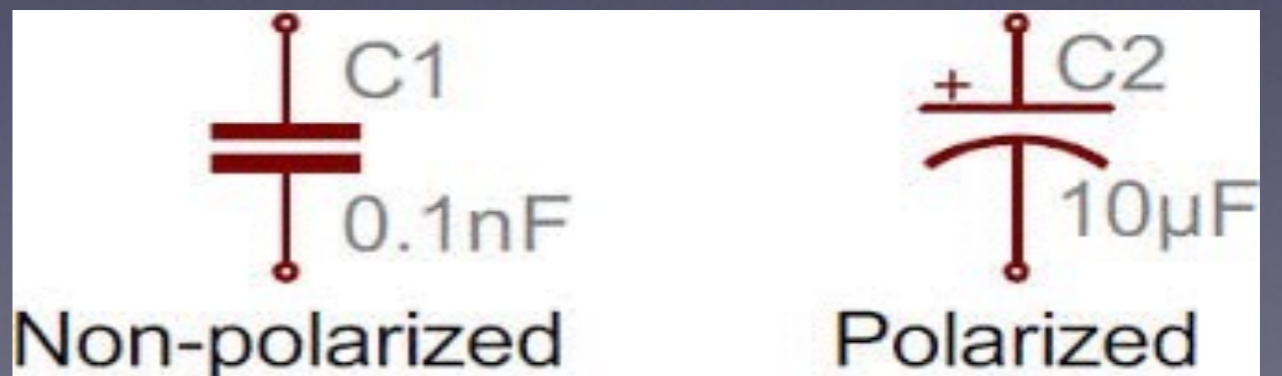
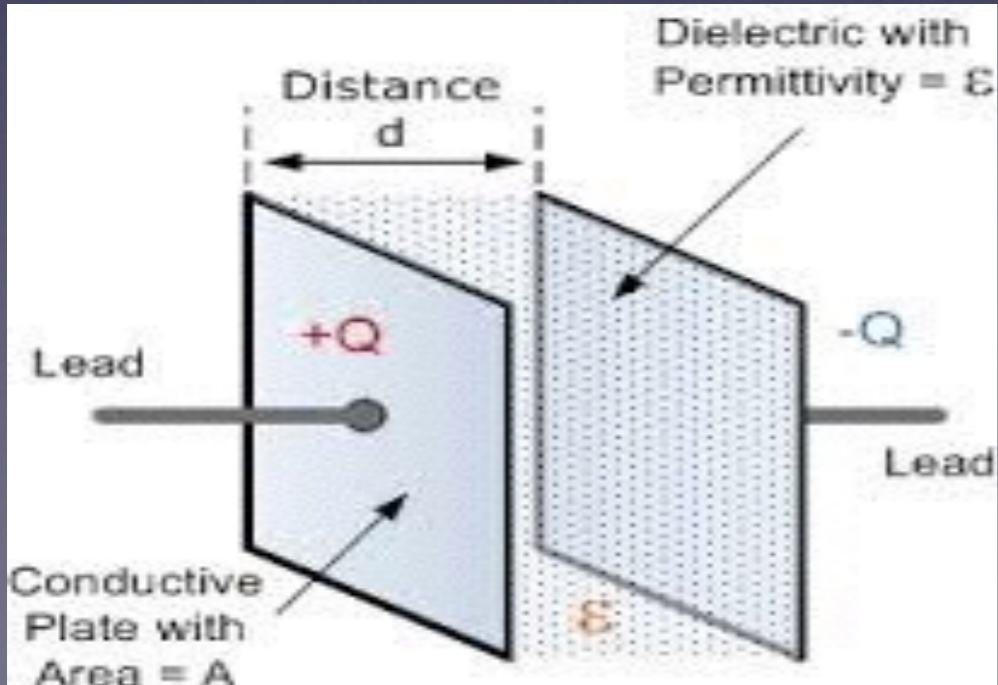
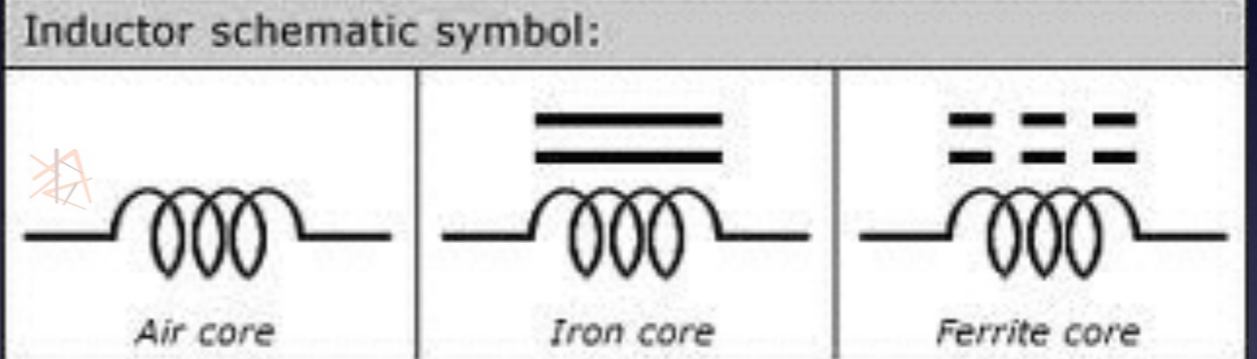
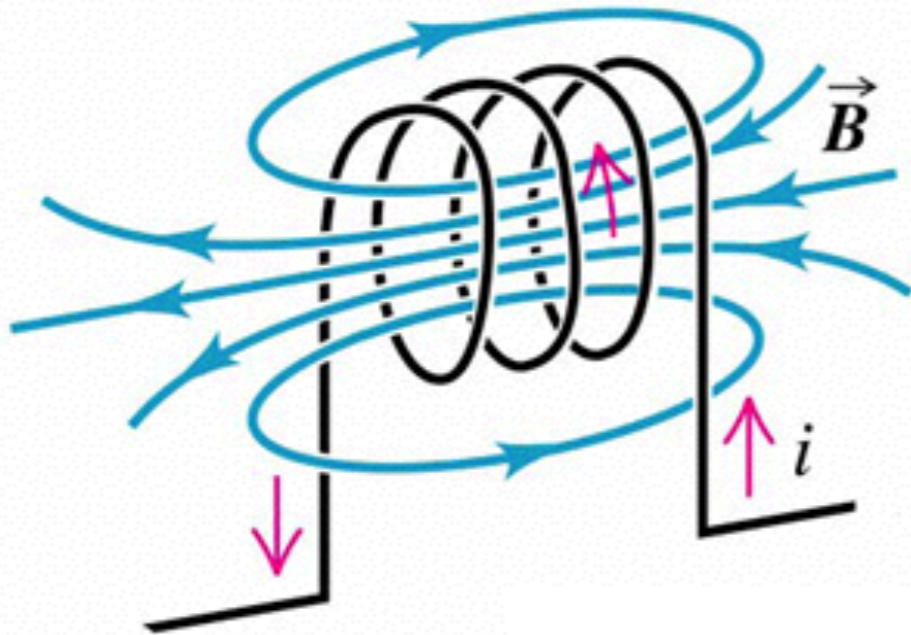




Figure 2.2 Electrons squeezing their way through a resistor.

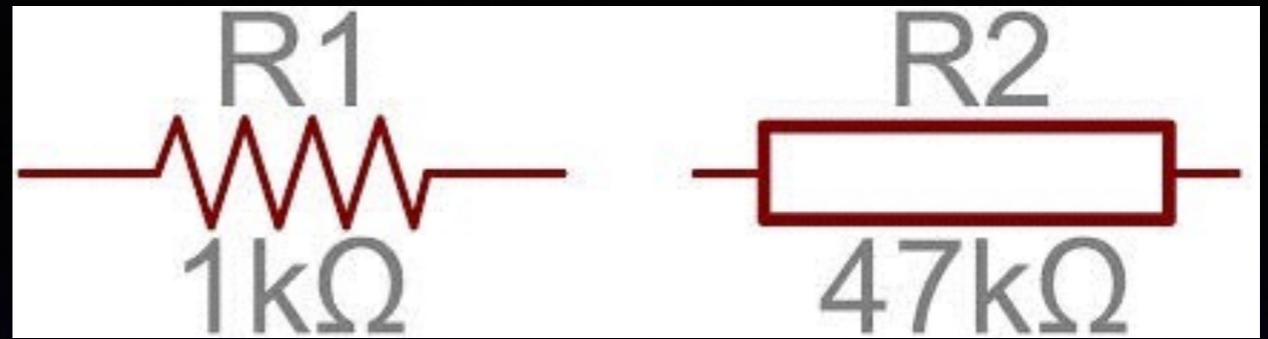

Elements

- Semiconductor
- In Periodic Table, Si is a very good element for making Semiconductors
- Semiconductors can have conductivity in specific conditions
- Si has four peripheral electrons
- 3족 원소 첨가시, P type Semiconductor 생성
- 5족 원소 첨가시, N type Semiconductor 생성

Elements

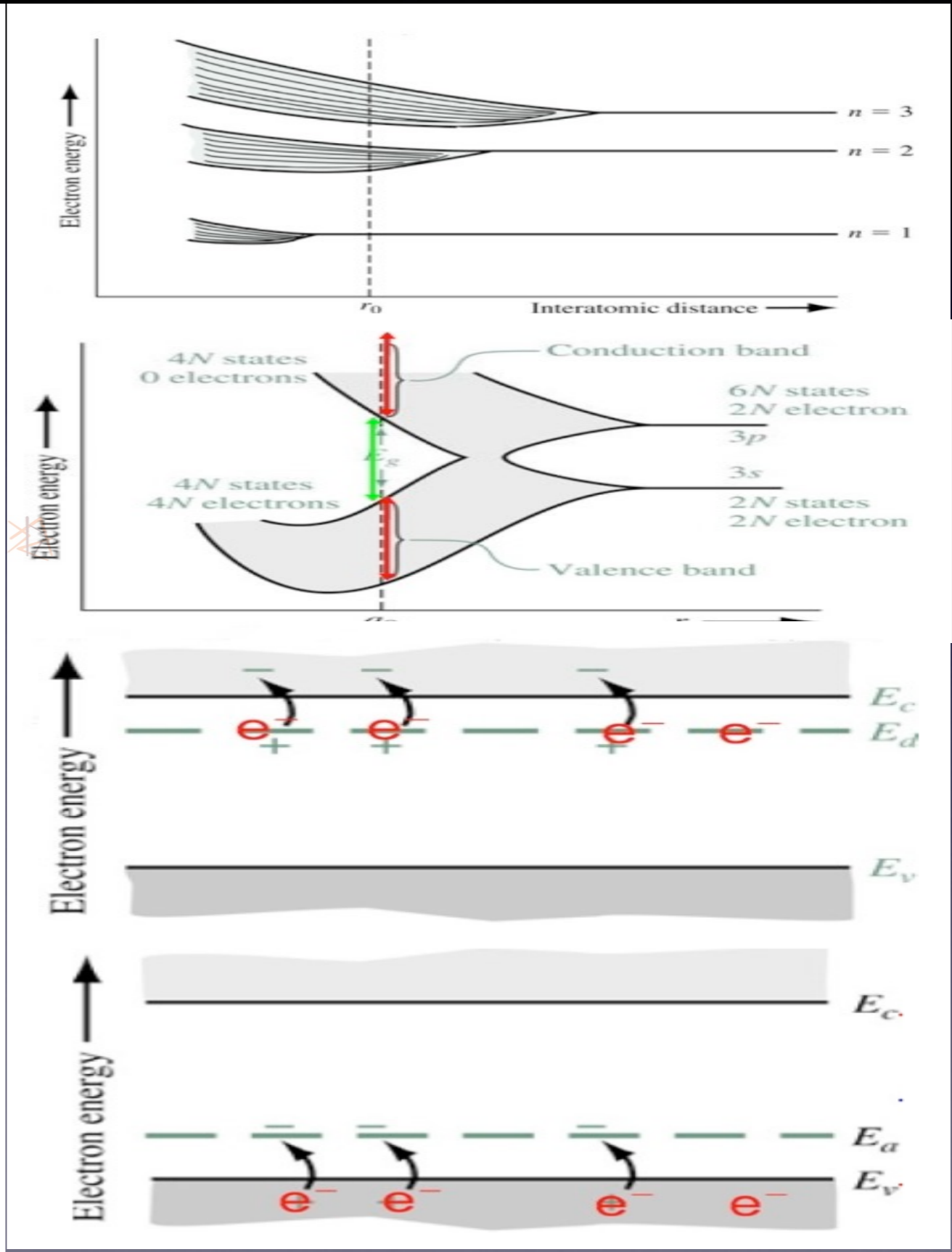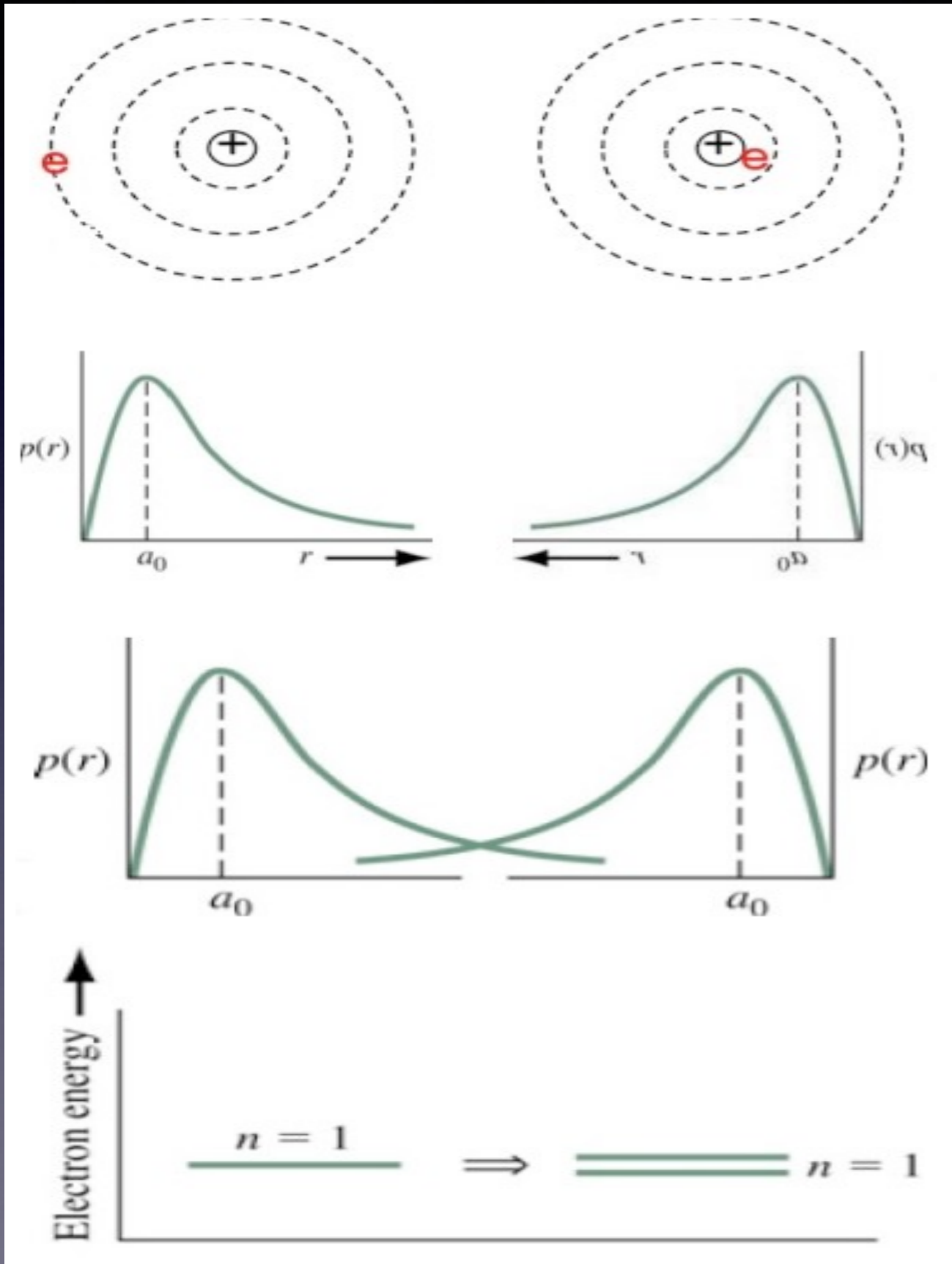



Elements

- Diode, Transistor
- By putting N-type and P-type Semiconductor together, they form a Diode(


P	d	N
---	---	---

)
- When 3 semiconductors are put together in forms of NPN or PNP, they form a Transistor (Bipolar Junction Transistor)
- MOSFET (Metal Oxide Semiconductor Field Effect Transistor) has a different structure

Elements

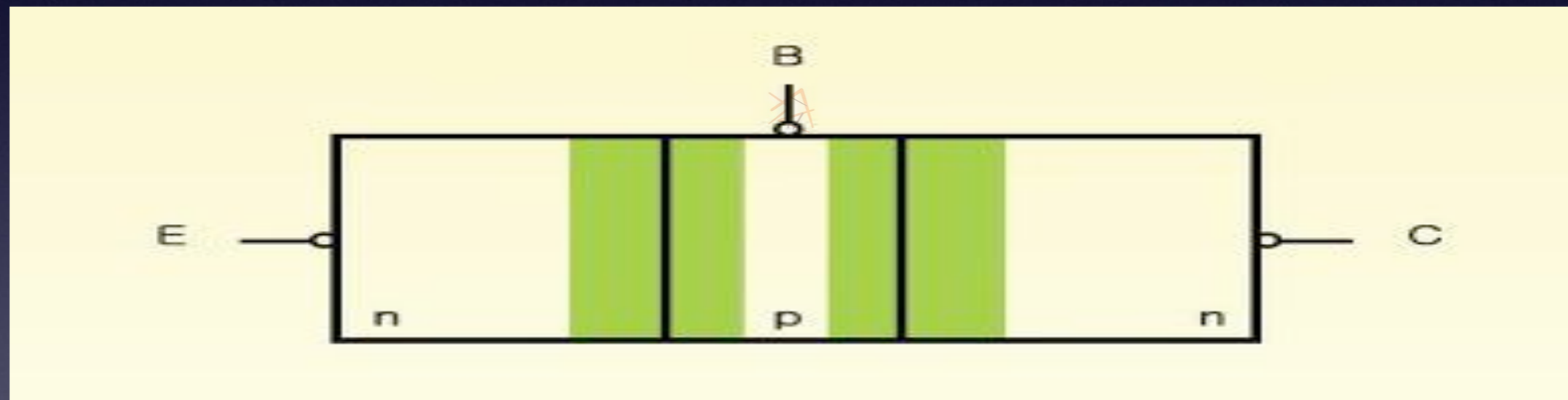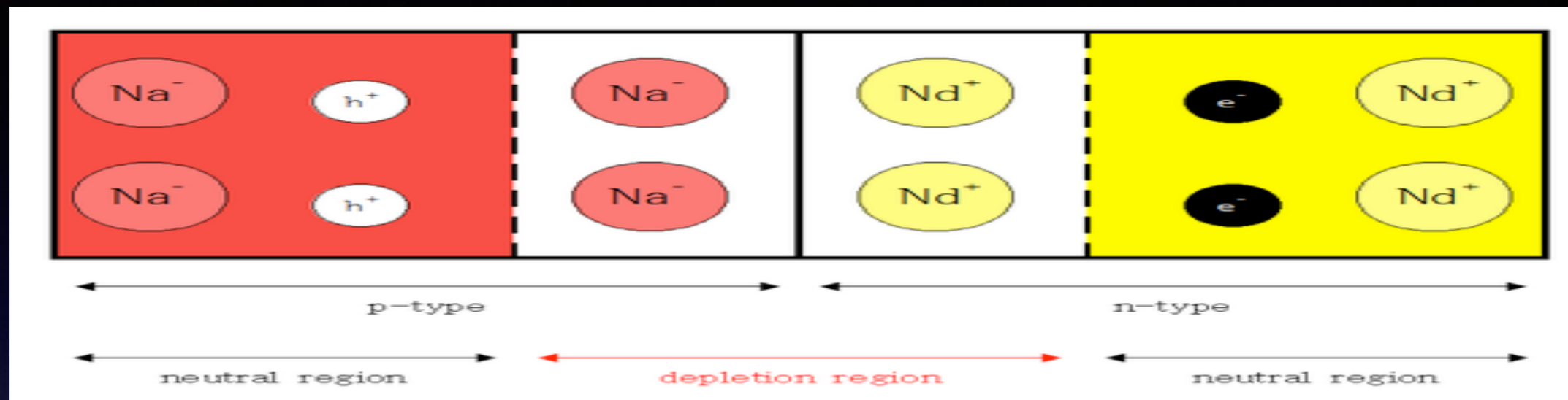

MOSFET

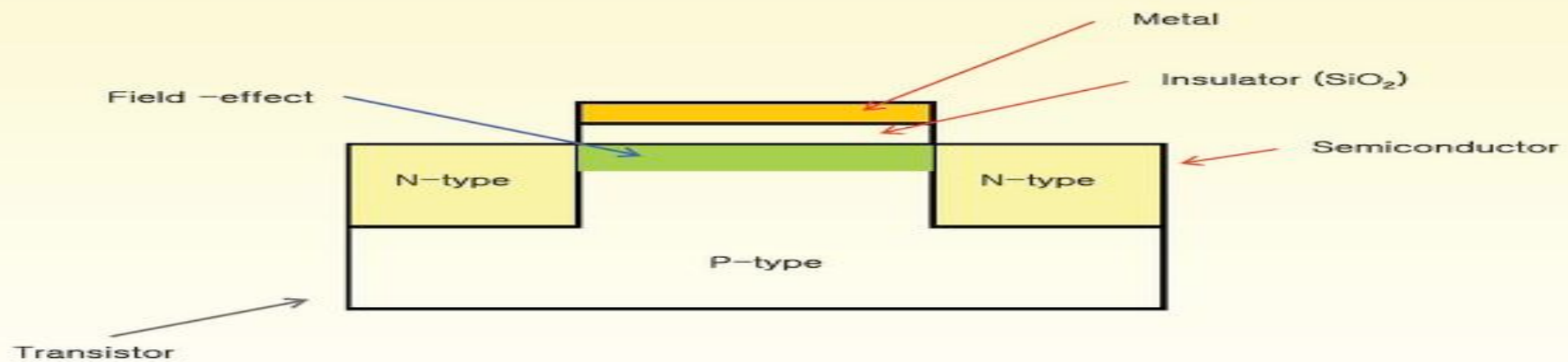

Elements

FET

낮은 전압이득
높은 전류이득
아주 높은 입력 임피던스
높은 출력 임피던스
노이즈를 적게 발생
스위칭 속도가 빠름
정전기에 약함
Gate로 0이 들어오면 ON 또는 OFF됨
전압에 의해 제어됨
BJT 보다 가격이 비싸다
바이어스 설정이 어렵다





BJT

높은 전압이득
낮은 전류이득
낮은 입력 임피던스
낮은 출력 임피던스
노이즈를 중간쯤 발생
스위칭 속도가 중간
정전기에 강함
Base로 0이 들어오면 OFF됨
전류에 의해서 제어됨
가격이 싸다
바이어스 설정이 쉽다.


Circuit Analysis

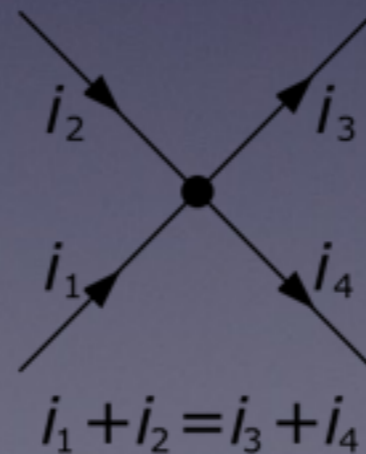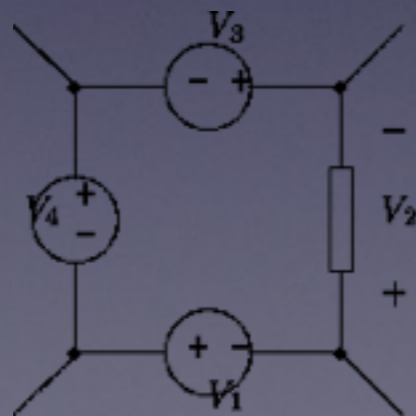- Basic Circuit Formula
- Ohm's Law : $V = IR$
- Kirchhoff's Voltage/Current Law



Circuit Analysis

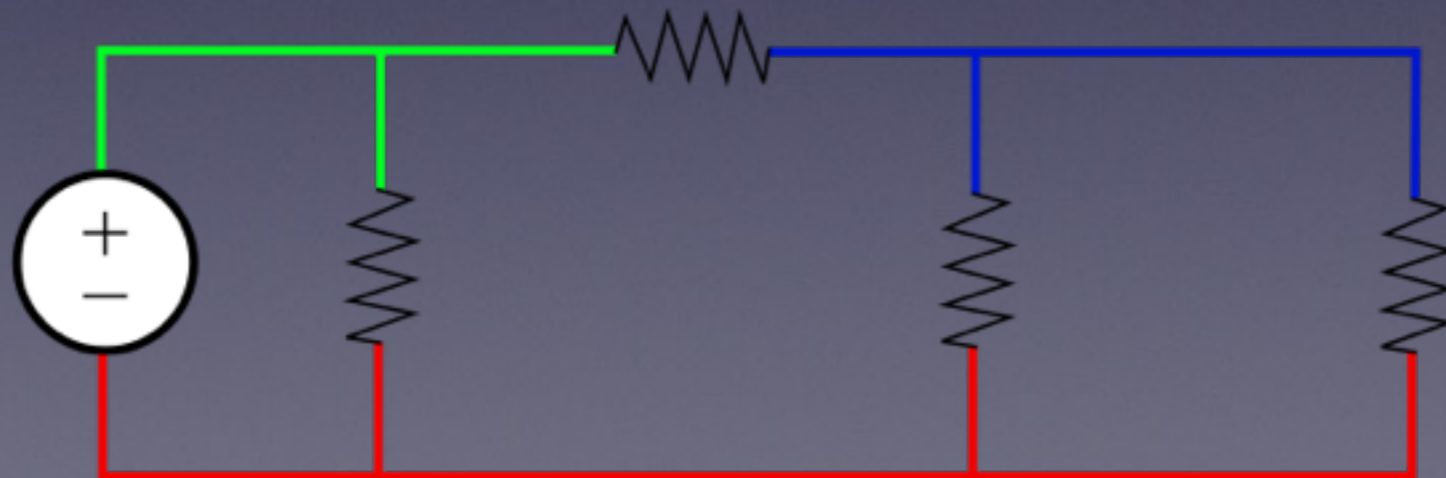- Node : 두 개 이상의 회로 요소가 만나는 지점
- Mesh : 회로에서의 하나의 폐루프
- Circuit Analysis : Node Voltage, Mesh Current, Supernode, Thevenin&Norton's Equivalent Circuit



Circuit Analysis


- In RLC Series Circuit, Let $V = V \cos(\omega t + \theta)$, $i = i \cos(\omega t + \theta)$
($\omega = 2 \cdot \pi \cdot f$)
- In Inductor, $V = L \cdot d(i \cos(\omega t + \theta))/dt = -\omega L \sin(\omega t + \theta) = -\omega L \cos(\omega t + \theta - 90)$
- By Euler Formula($e^{\pm j\theta} = \cos\theta \pm j\sin\theta$)
- $V = -\omega L i e^{j(\theta - 90)} = j\omega L i e^{j\theta}$ ($\because \cos 90 = 0, \sin 90 = 1$)
- Thus, $V = j\omega L \cdot i$ ($i e^{j\theta} = i$)

Circuit Analysis

- In Capacitor $i = C \cdot d(V\cos(\omega t + \theta))/dt = -C \cdot \omega V \sin(\omega t + \theta) = -\omega C V \cos(\omega t + \theta - 90)$
- By Euler Formular, $i = -\omega C V e^{j(\theta - 90)} = j\omega C V e^{j\theta}$
- Thus, $V = \frac{1}{j\omega C} i$

Circuit Analysis

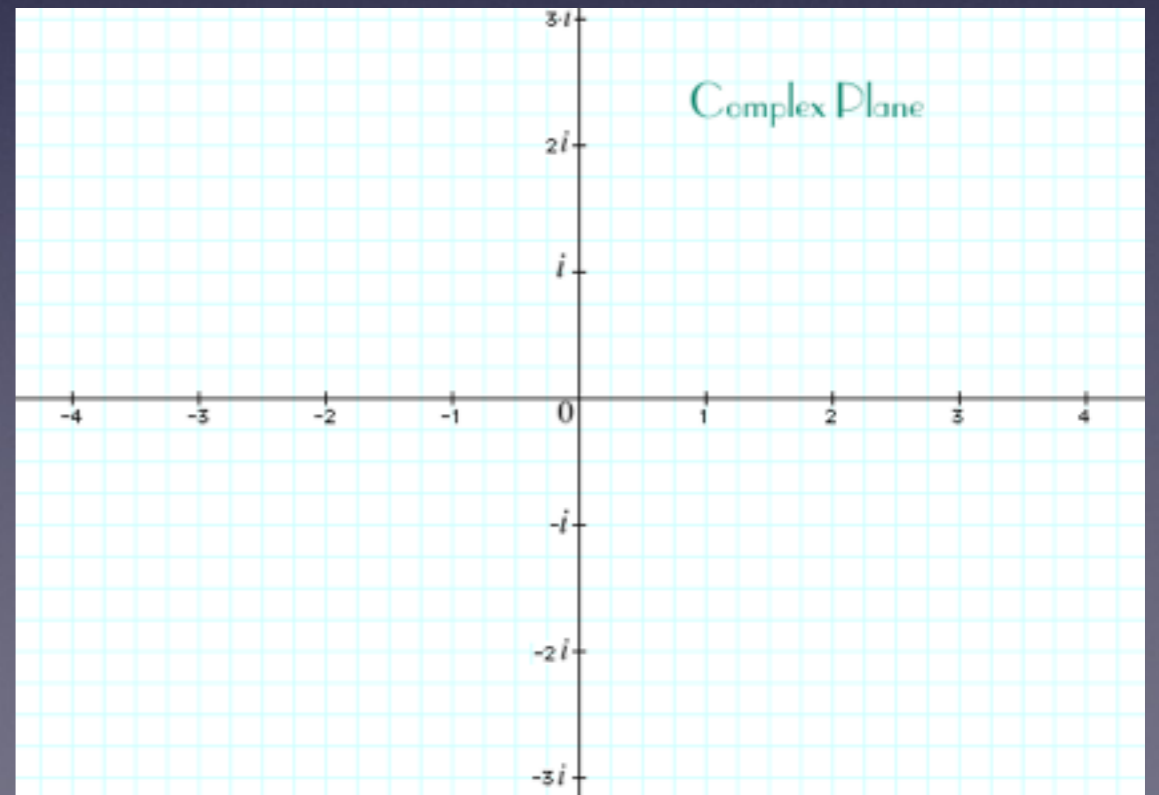- For each Elements
- Resistor : $V= Ri$
- Inductor : $V= (j\omega L) \cdot i$
- Capacitor : $V = (1/j\omega C) \cdot i$
- Why Complex Number? : Phase!



Circuit Analysis


	Impedence(Z)	Reactance(X)
Resistor	R	R
Inductor	$j\omega L$	ωL
Capacitor	$1/j\omega C$	$1/\omega C$

Circuit Analysis

- 기타 회로해석 기법
- Laplace Transformation(s-domain Circuit Analysis)
- Fourier Transformation(f-domain Circuit Analysis)
- s-domain \rightarrow Transfer function for Circuit Stability
- f-domain \rightarrow Frequency Response



Analog VS Digital

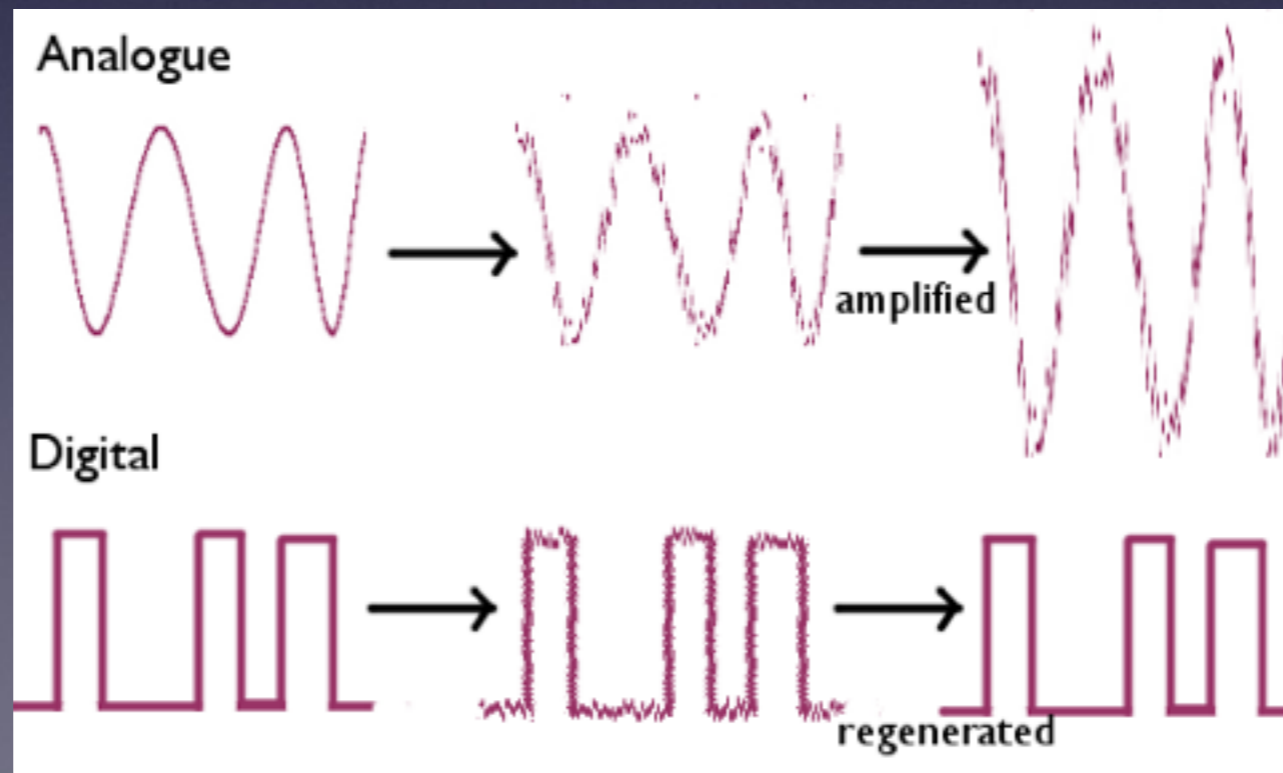- Analog : Continuous
- Digital : Discontinuous
- Main difference : Noise Immunity




Application Of Element

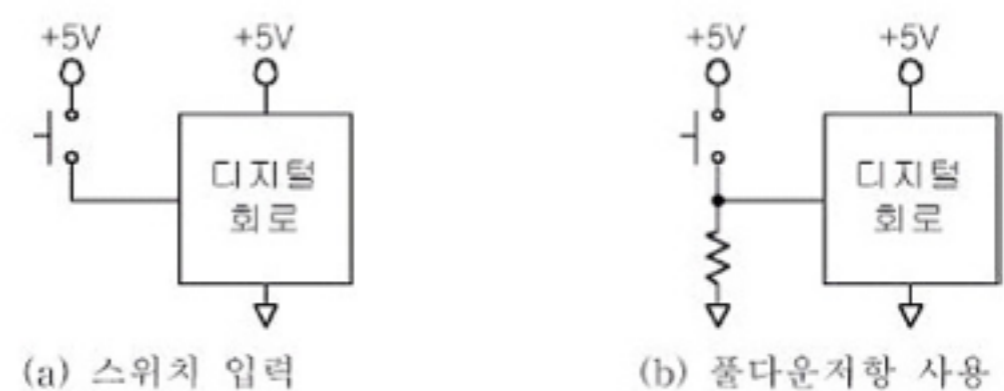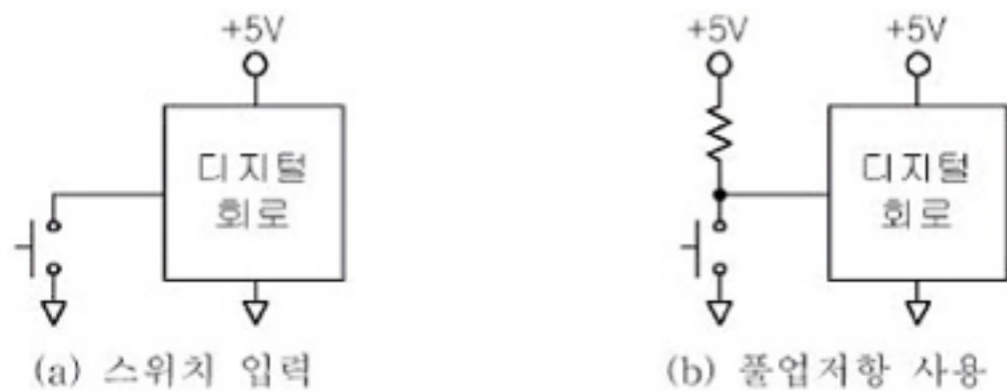- Pull Up/Down Resistor
- Current Flow to Low Resistor
- Digital Signal has two condition : High / Low
- With Pull up or Pull down Resistor, We can easily define Digital Signal Condition



Application Of Element

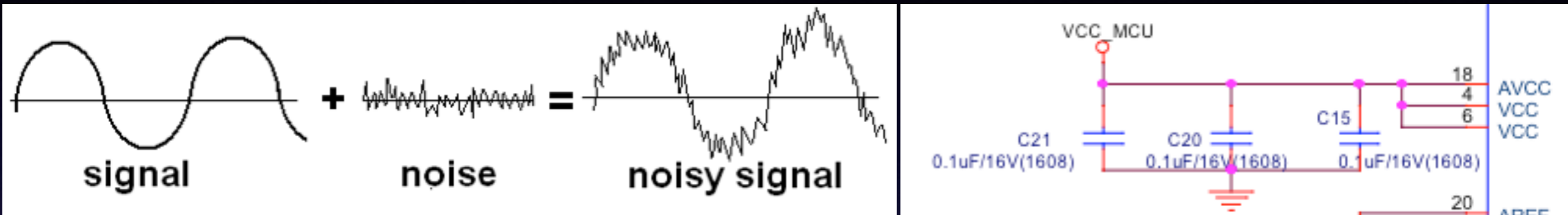

- Bypass Capacitor
- In Capacitor, X_c is $1/\omega C$
- if frequency goes high \rightarrow X_c goes to zero
- All high frequency signals easily pass Capacitor

Application of Element

- Bead(Not Inductor, But Very Similar)
- Digital Signal has a very high frequency when compared to Analog Signal
- In Inductor, Reactance is ωL
- High frequency cannot pass Inductor(Reactance goes to infinity)
- Easily Separate Analog and Digital Signal

Application of Element

	Reactance	High Frequency	Low Frequency
Resistor	R	–	–
Capacitor	$1/\omega C$	Short	Open
Inductor	ωL	Open	Short

Open : Signals cannot flow / Short : Flow with no obstacle

Application of Element

- TTL(Transistor-Transistor Logic)
- CMOS (Complementary Metal Oxide Semiconductor)
- 논리 게이트(AND, OR, NOT, NAND, NOR) 제작에 응용
- TTL 동작 전압 : 5V, 출력전류 20mA(Typ.)
- CMOS 동작 전압 : 3.3V, 출력전류 10mA(Typ.)
- BJT Collector Current : $I_c = A J_s [e^{V_{BE}/V_t} - 1]$
- MOSFET Drain Current : $I_D = \mu C_{ox} \frac{W}{L} (V_{GS} - V_T) V_{DS}$

Block Diagram

- H/W System has a typical structure



Block Diagram

- Input : Sensor, Switch, MIC, etc
- Control : MCU, DSP, MPU
- Output : LCD, Speaker, LED, etc
- Determine How to Connect/Control each device

Design H/W System

- Datasheet : All device/element have datasheet
- Datasheet has all information about its device/element
- Absolute Maximum Ratings, DC/AC Characteristics, Pin Assignment, Resister Map, Reference Design
- Design H/W System \Leftrightarrow 데이터시트 분석

이 세미나는 다음과 같이 진행되었습니다
우선적으로 하드웨어 개발에 있어서 가장 필수적인 회로 소자들을 소개하고 그 소자(Element)가 어떤 역할을 하는지에 대해 설명했습니다.

그 후 회로를 통과하는 신호를 두 가지로 나누어서 설명하고 두 신호의 제어에 있어서 위에 설명한 소자들이 이 신호제어에 있어서 어떻게 응용이 되는지 실무와 연관해서 설명하였습니다

최종적으로 이 이론들을 가지고 하드웨어를 설계/개발함에 있어서 추가적으로 필요한 부분들을 소개하고 실제로 제가 개발하는 제품에 어떻게 응용했는지를 설명을 했습니다

그 예를 제가 개발중인 Wand로 설명했는데, 회사 개발자분들과의 세미나다 보니 모든 소스와 설계도를 오픈했지만, 블로그에 올리기에는 적합하지 않다 생각하여 아예 삭제하였습니다